

Transistor Suggestion

- ① why is a transistor so called?
- ② Explain with diagram the different current components in a transistor.
- ③ Define the terms
 - i) Emitter injection ratio
 - ii) Base transport factor.

Hence derive the relationship between the current gain in common emitter (CE) and CB mode (i.e. β and α).

- ④ Explain early effect in a transistor.
- ⑤ Compare CE and CB and CC Configuration.
- ⑥ write short note on transistor as a switch.

- ⑦ What is the need for biasing?
- ⑧ What are the reasons for shift of Q-point?
- ⑨ Develop the H-parameter model of a transistor, why is it called the small signal equivalent model?
- ⑩ Derive expression for stability factor S_{WIB} in self bias voltage divider configuration.
- ⑪ Find expression for voltage gain, current gain, input impedance and output impedance in terms of H-parameters.
- ⑫ Explain physically how
(a) Collector to Base Bias
(b) Self Bias achieve stability

13) Explain what happens if the collector resistance in a common emitter circuit is increased indefinitely (Transistor)