



# Transistor Modeling


By

**Dr. ANUPAM KARMAKAR**

Associate Professor & Head

Department of Electronic Science

University of Calcutta

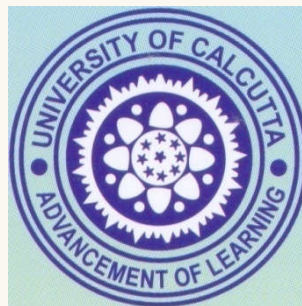

[akelc@caluniv.ac](mailto:akelc@caluniv.ac), [akarmakar.cu@gmail.com](mailto:akarmakar.cu@gmail.com)



# Introduction

- For the analysis of **small**-signal AC response of BJT amplifier the knowledge of modeling the transistor is important.
- The input signal will determine whether it's a **small**-signal (AC) or **large** signal (DC) analysis.
- The goal when modeling **small**-signal behavior is to make of a transistor that work for **small**-signal enough to “keep things linear” (i.e., not to distort too much).
- There are two models commonly used in the small-signal analysis:
  - (a)  $r_e$  model
  - (b) hybrid equivalent model

## Disadvantages

$r_e$  - model : Fails to account the output impedance level of device and feedback effect from output to input.


Hybrid equivalent model : Limited to specified operating condition in order to obtain accurate result.


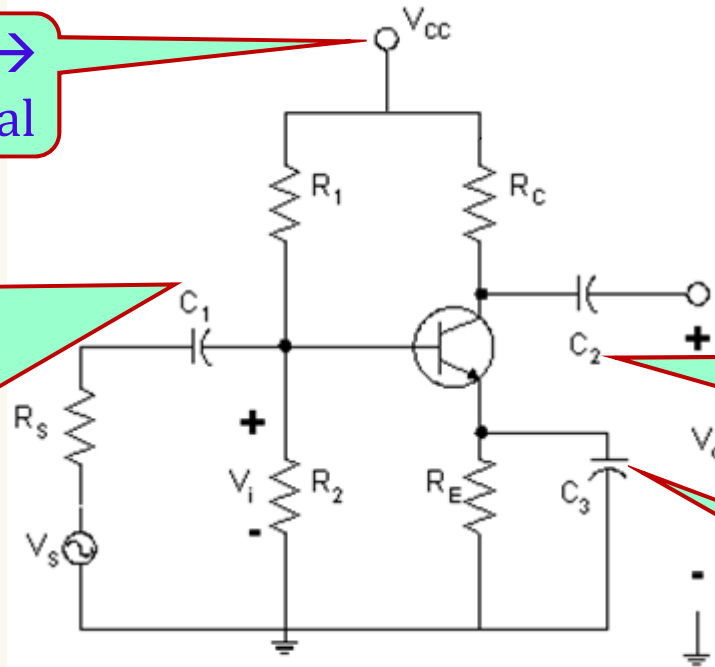
# CB-mode: Voltage-divider Configuration under AC analysis

DC supply  $\rightarrow$   
"0" potential


- I/p coupling capacitor  $\rightarrow$  s/c
- Large values
- Block DC and pass AC signal





- O/p coupling capacitor  $\rightarrow$  s/c
- Large values
- Block DC and pass AC signal

- Bypass capacitor  $\rightarrow$  s/c
- Large values

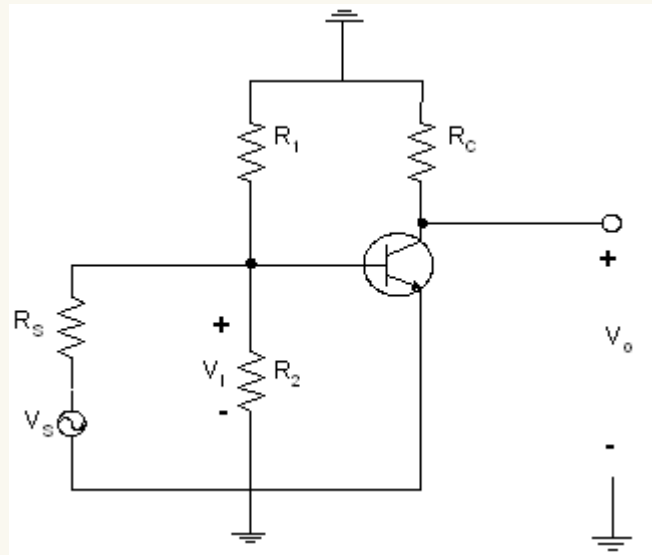Redrawn voltage-divider configuration after removing dc supply and inserting s/c for the capacitors


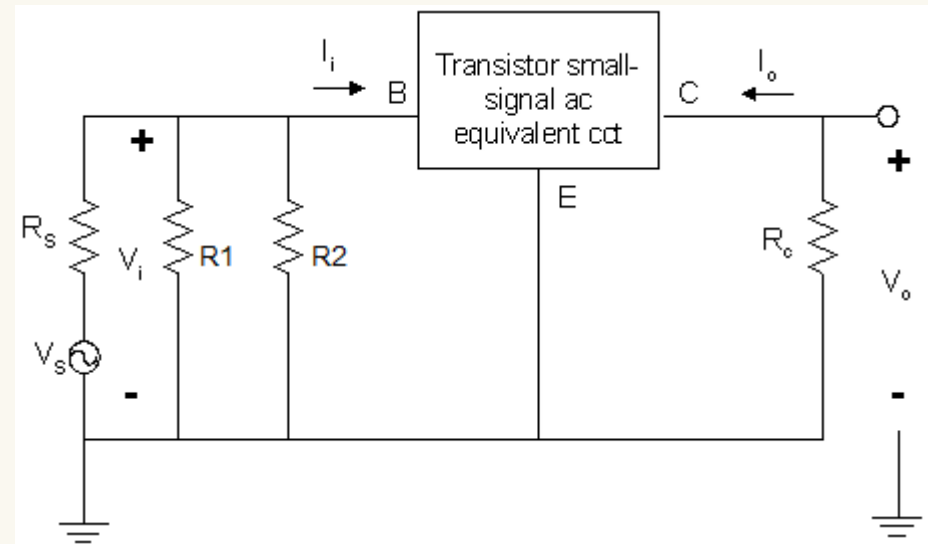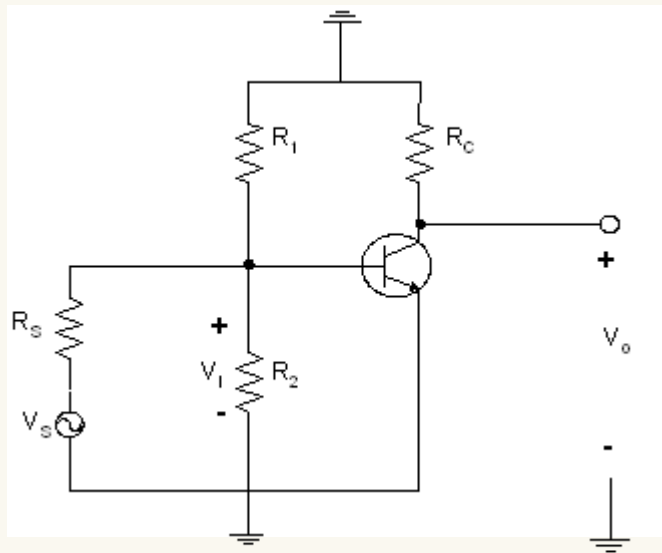
# Transistor Small-Signal AC Equivalent Circuit



Redrawn voltage-divider configuration after removing dc supply and inserting s/c for the capacitors

Redrawn for small-signal AC analysis

## AC Analysis:

- (1) Replace all DC sources by ground.
- (2) Coupling and Bypass capacitors are short ckt. The effect of there capacitors is to set a lower cut-off frequency for the ckt.
- (3) Inspect the ckt. (replace BJTs with its small signal model :  $r_e$  or hybrid).
- (4) Solve for voltage and current transfer function, i/o and o/p impedances.



# The $r_e$ – Transistor Model

- Small-signal  $r_e$  – model of transistor is simple.
- It employs a diode and controlled current source to depict the behavior of a transistor in the region of interest.
- Output characteristics reveal that BJT amplifiers are referred to as current-controlled devices.
- In the active region of operation of a transistor, emitter-base junction is forward biased and collector-base junction is reverse biased.

# The $r_e$ - Transistor Model

## Common-Base Configuration:

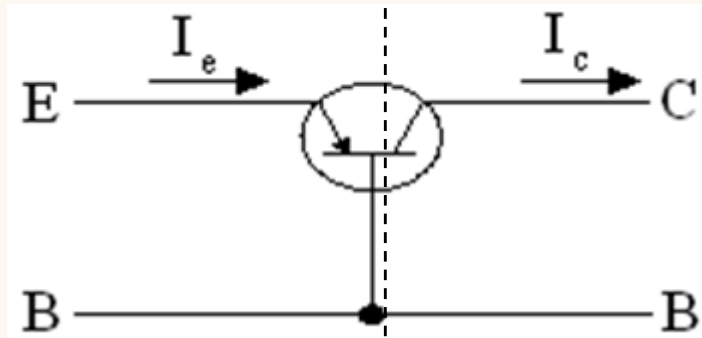


Fig. (b): CB *pnp* transistor.

- The straight line-segment of input characteristics (Fig. b) of BJT in active region portrays that the forward biased emitter-base junction (input side) of the transistor resembles with that of a forward biased diode (Fig. c).

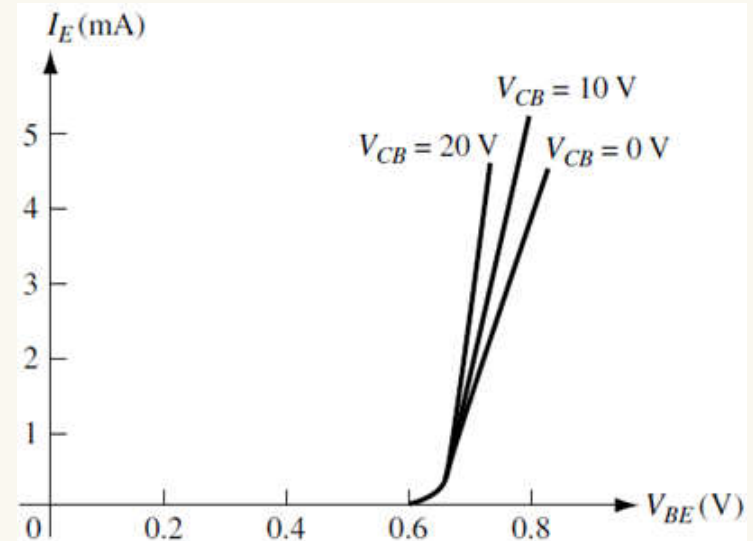


Fig. (b): CB *pnp* transistor input characteristics.

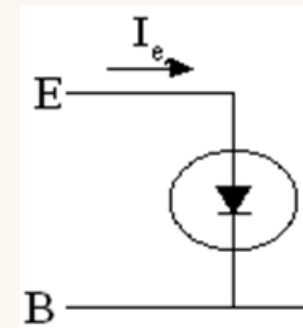


Fig. (c): Equivalent circuit of input side.

# The $r_e$ - Transistor Model: Common-Base Configuration

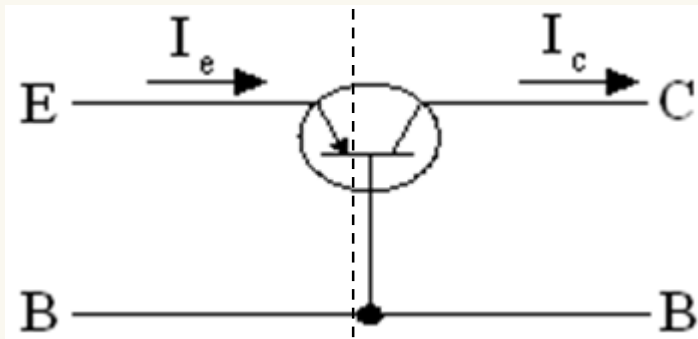


Fig. (a): CB *pnp* transistor.

- The straight line-segment of output characteristics (Fig. b) of BJT in active region portrays that the collector-base junction (output side) of the transistor resemble with that of a constant current source (Fig. c).

- The current source in Fig. (c) establishes the fact that the output current  $I_c = \alpha I_e$ , depends on the controlling current  $I_e$ , the emitter (input) current in the input side.

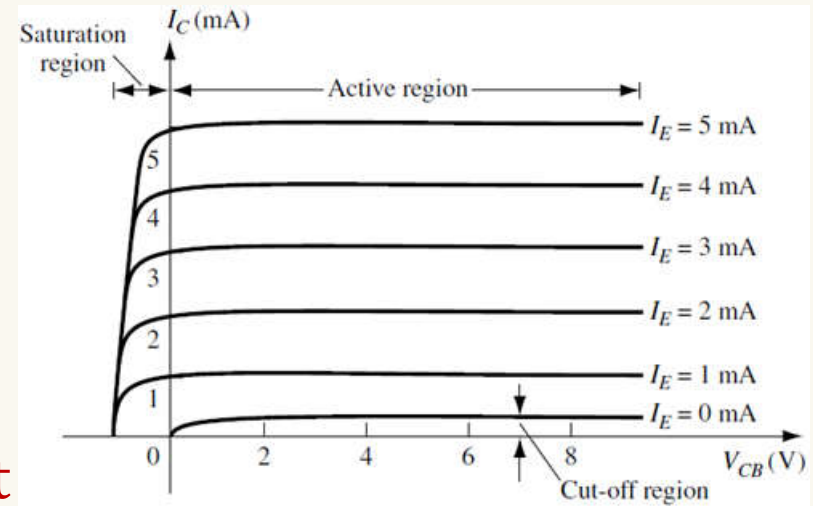


Fig. : CB *pnp* transistor output characteristics.

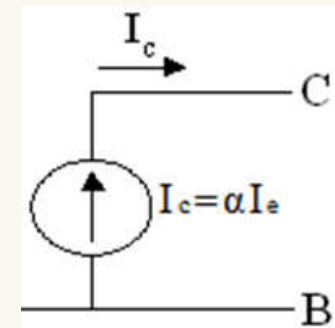


Fig. (c): Equivalent circuit of output side.

# The $r_e$ – Transistor Model: Common-Base Configuration

- Therefore the equivalence at the input-output terminals with the current-controlled source, providing a link between the two have been established as depicted in Fig. (a).

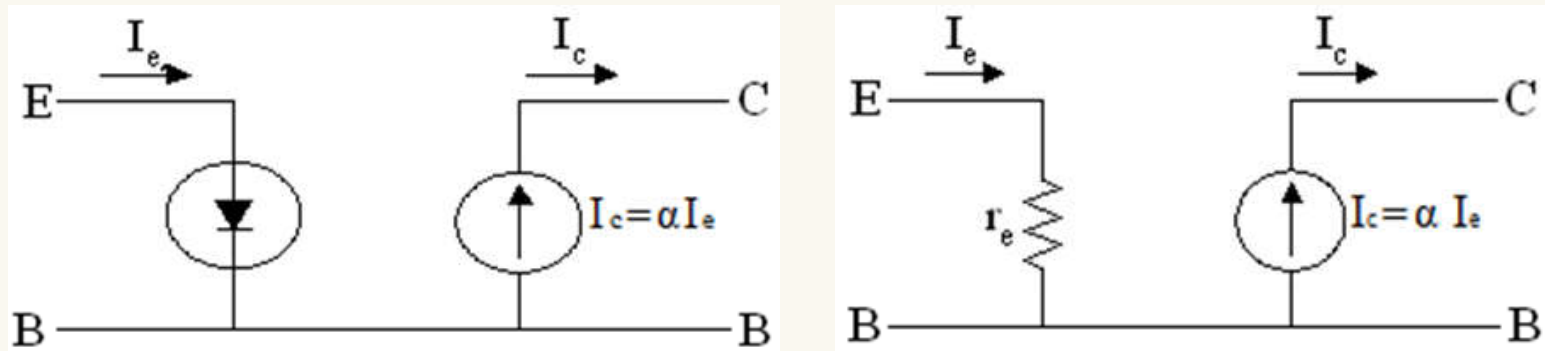


Fig. (a):  $r_e$  – model of transistor in CB configuration.

- Forward resistance of a diode is determined by  $r_{ac} = \frac{26 \text{ mV}}{I_d} \Omega$ , where  $I_d$  is the diode current at the  $Q$ -point.
- In CB transistor configuration, the diode current is emitter current  $I_E$ , thus the notation of the diode resistance is  $r_e$  and its value is given by

$$r_e = \frac{26 \text{ mV}}{I_E} \Omega$$



# The $r_e$ – Transistor Model

## Common-Emitter Configuration:

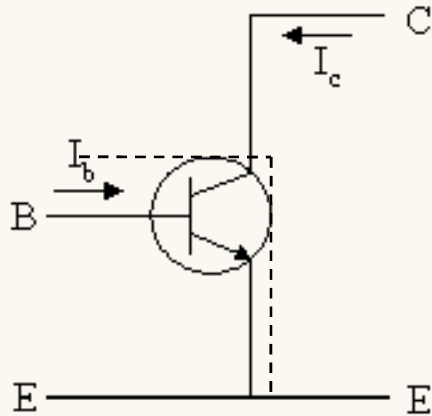


Fig. (a): CE *n*p*n* transistor.

- The straight line-segment of input characteristics (Fig. b) of BJT in active region portrays that the forward biased emitter-base junction (input side) of the transistor resembles with that of a forward biased diode (Fig. c).

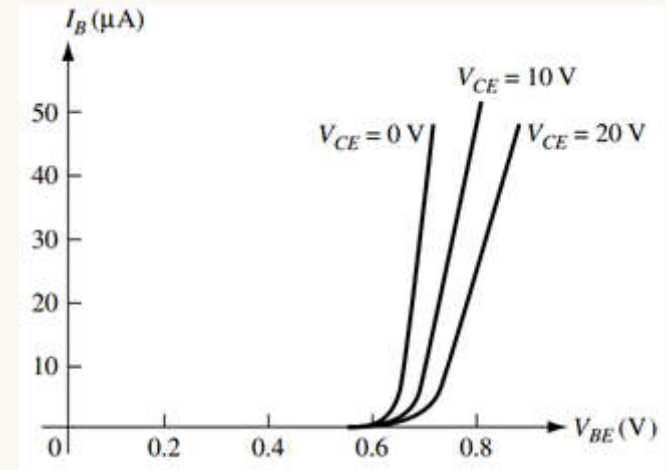


Fig. (b): CE *n*p*n* transistor input characteristics.

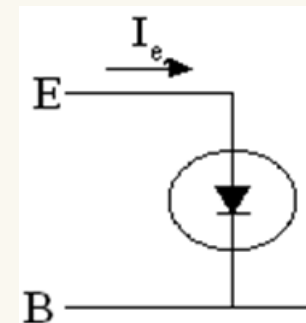


Fig. (c): Equivalent circuit of input side.

# The $r_e$ – Transistor Model

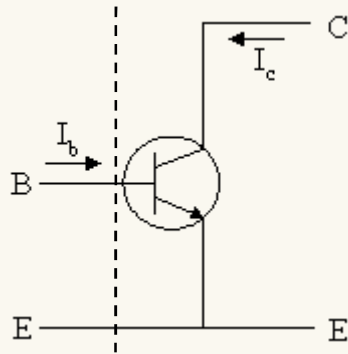


Fig. (a): CE *nnp* transistor.

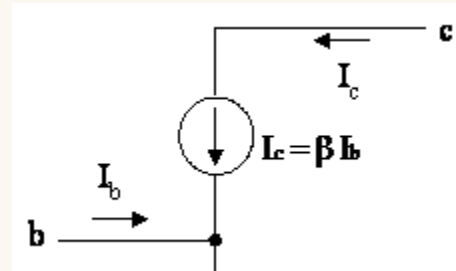


Fig. (c): Equivalent circuit of output side.

- The straight line-segment of output characteristics (Fig. b) of BJT in active region portrays that the collector-emitter terminals (output side) of the transistor resemble with that of a constant current source (Fig. c).

- The current source in Fig. (c) establishes the fact that the output current  $I_C = \beta I_B$ , depends on the controlling current  $I_B$ , the base (input) current in the input side.

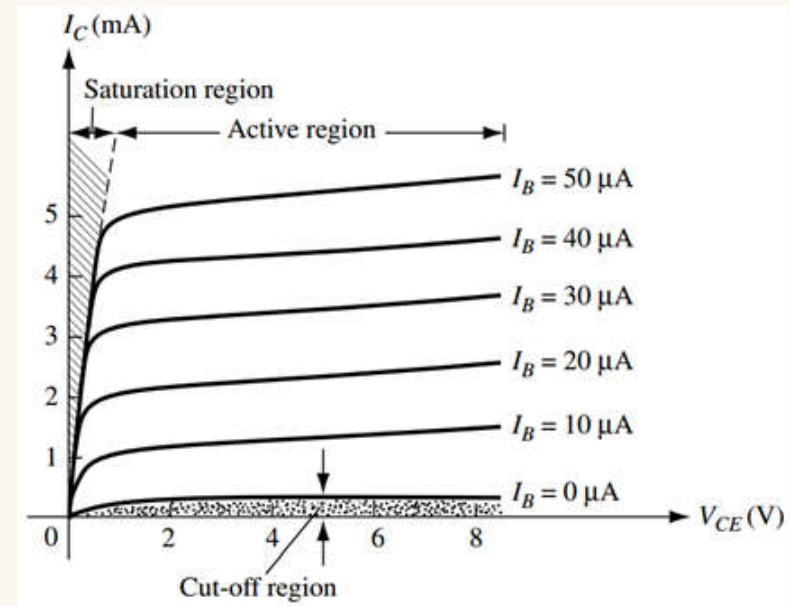


Fig. : CB *pnp* transistor output characteristics.

# The $r_e$ - Transistor Model

- Therefore the equivalence at the input-output terminals with the current-controlled source, providing a link between the two has been established as depicted in Fig. (a).

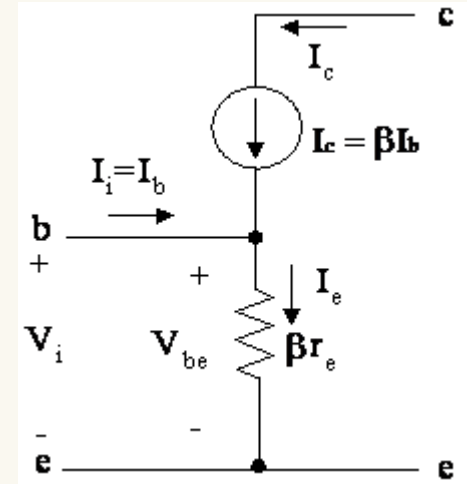
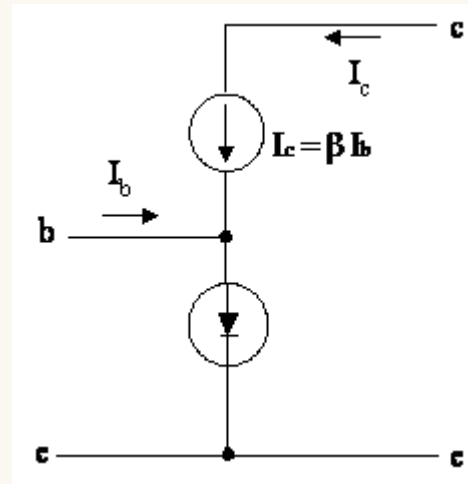


Fig. (a):  $r_e$  - model of transistor in CE configuration.

- In CE configuration,  $I_C = \beta I_B$ .

Hence, current through the diode is given by

$$I_E = I_C + I_B = \beta I_B + I_B = (\beta + 1)I_B \approx \beta I_B.$$

- Thus, the ac resistance of the diode is given by

$$r_{ac} = \frac{26 \text{ mV}}{I_B} = \frac{26 \text{ mV}}{I_E / \beta}$$

$$\text{or, } r_{ac} = \beta \frac{26 \text{ mV}}{I_E} = \beta r_e$$

# The $r_e$ - Transistor Model

- Close examination of output characteristics of CE transistor configuration reveals that the slope of the curves increases with increase in collector current. The steeper the slope, the less the level of output impedance ( $r_o$ ) between the collector and emitter terminals as shown in Fig.


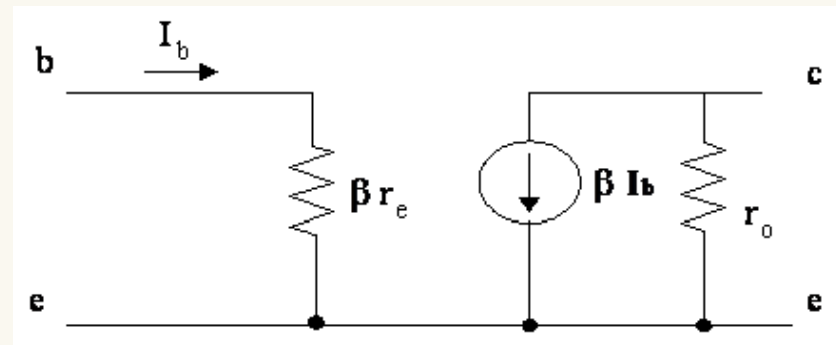


Fig. (a):  $r_e$ - model of transistor in CE configuration.

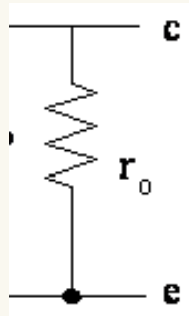- Considering the fact that the resistance between the base and emitter terminal is  $\beta r_e$ , the collector current is  $\beta I_b$ , and the output resistance is  $r_o$ , the equivalent  $r_e$  - model of a transistor in CE configuration can be depicted as in Fig.



# Forward Biased Diode Resistance

- Diode current is given by

$$I_d = I_S(e^{kT/V} - 1)$$

- where,  $I_S$  is reverse saturation current,  $k$  = Boltzmann's constant,  $V$  = voltage across the forward biased diode,  $T$  = temperature in K.
- Taking derivative w.r.t. the applied bias, results in

$$\frac{d(I_d)}{dV} = \frac{d}{dV} [I_S(e^{kT/V} - 1)]$$

$$\text{or, } \frac{dI_d}{dV} = \frac{k}{T} I_S e^{kT/V} = \frac{k}{T} (I_d + I_S) \cong \frac{k}{T} I_d$$

- At room temperature,  $T = 25 + 273 = 298$  K, and then substituting  $k = 11,600$ , yields

$$\frac{dI_d}{dV} = \frac{11600}{298} I_d \cong 38.93 I_d$$

- Therefore, the diode ac resistance can be determined as

$$r_d = \frac{dV}{dI_d} = \frac{1}{38.93 I_d} = \frac{0.026}{I_d} = \frac{26 \text{ mV}}{I_d}$$

# Hybrid-Parameters Model


By

**Dr. ANUPAM KARMAKAR**

Associate Professor & Head

Department of Electronic Science

University of Calcutta

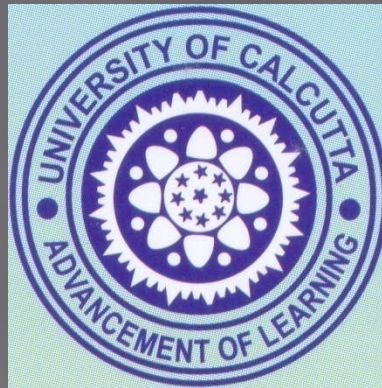

**<akelc@caluniv.ac, akarmakar.cu@gmail.com>**



# Hybrid-Parameters Model



For the basic three terminal devices, there are two ports (pair of terminals), the input terminals at the left and output terminals at the right. Four variables are related by the equations:


$$\begin{aligned} V_i &= f(I_i, V_o) \\ I_o &= f(I_i, V_o) \end{aligned}$$

$$V_i = h_{11}I_i + h_{12}V_o \quad \dots \dots (1a)$$

$$I_o = h_{21}I_i + h_{22}V_o \quad \dots \dots (1b)$$

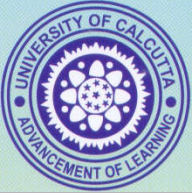The parameters relating the four variables are called *h-parameter* from the word 'hybrid', because of the mixture of variables (*V* and *I*) in each equation results in a 'hybrid' set of units of measurement for the *h*-parameters





# $h$ -Parameters

If in (1a),  $V_o$  is set to zero by short-circuiting the output terminals, then

$$h_{11} = h_i = \left. \frac{V_i}{I_i} \right|_{V_o=0} \quad \dots \quad (2a)$$

The ratio (2a) indicates that  $h_{11}$  is an impedance parameter to be measured ohm ( $\Omega$ ). Since  $h_{11}$  ( $h_i$ ) is the ratio of *input* voltage to *input* current with output terminals *shorted*, so it is called ***short-circuit input impedance*** parameter.

If in (1a),  $I_i$  is set to zero by opening the input terminals, then

$$h_{12} = h_r = \left. \frac{V_i}{V_o} \right|_{I_i=0} \quad \dots \quad (2b)$$

The ratio (2b) indicates that  $h_{12}$  is a unit less ratio of voltage parameter. Since  $h_{12}$  ( $h_r$ ) is the ratio of *input* voltage to *output* voltage with input terminals *open*, so it is called ***open-circuit reverse voltage gain*** parameter.



# $h$ -Parameters

Since each term of (1a) has the unit of volt, let the *Kirchhoff's voltage law* is applied in reverse, resulting in the circuit of Fig.

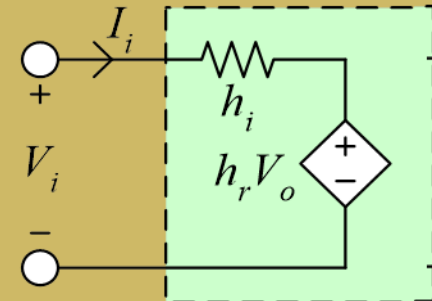


Fig. :  $h$ -parameter equivalent circuit of eq. (1a).

If in (1b),  $V_o$  is set to zero by short-circuiting the output terminals, then

$$h_{21} = h_f = \left. \frac{I_o}{I_i} \right|_{V_o=0} \dots (2c)$$

The ratio (2c) indicates that  $h_{21}$  ( $h_f$ ) is a unit less ratio of *output* current to *input* current with output terminals *shorted*, so it is called ***short-circuit forward current gain*** parameter.

# $h$ -Parameters

If in (1b),  $I_i$  is set to zero by opening the input terminals, then

$$h_{22} = h_o = \left. \frac{I_o}{V_o} \right|_{I_i = 0} \dots (2d)$$

The ratio (2d) indicates that  $h_{12}$  is an admittance parameter to be measured mho ( $\Omega$ ) or siemen (S).

Since  $h_{22}$  ( $h_o$ ) is the ratio of *output* current to *output* voltage with input terminals *open*, it is called ***open-circuit output admittance*** parameter.

Since each term of (1b) has the unit of current, let the *Kirchhoff's current law* is applied in reverse, resulting in the circuit of Fig.

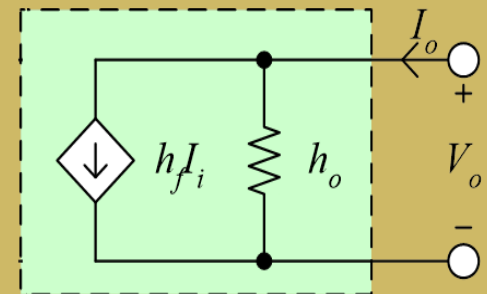


Fig. :  $h$ -parameter equivalent circuit of eq. (1b).

# $h$ -Parameter Model

Thus, the complete equivalent circuit for the basic three terminal linear devices is shown in Fig.

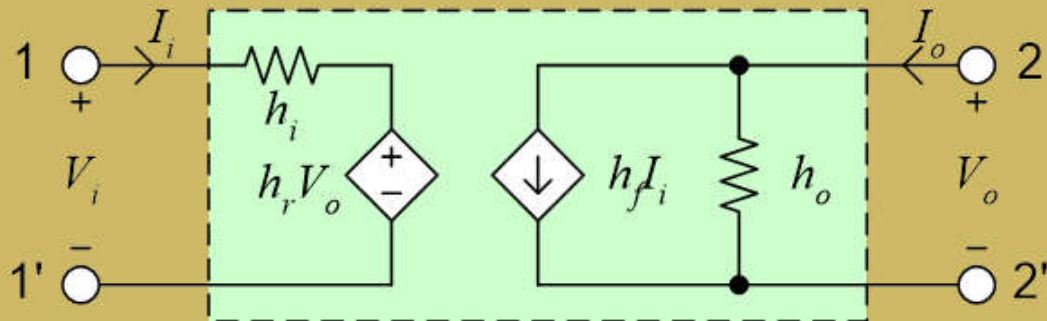


Fig. : Complete hybrid equivalent circuit.

$$V_i = h_{11}I_i + h_{12}V_o = h_i I_i + h_r V_o$$

$$I_o = h_{21}I_i + h_{22}V_o = h_f I_i + h_o V_o$$



$$h_{11} = \text{input impedance} = h_i$$

$$h_{12} = \text{reverse voltage gain} = h_r$$



$$h_{21} = \text{forward current gain} = h_f$$

$$h_{22} = \text{output admittance} = h_o$$



## CE $h$ -Parameter Equivalent Circuit

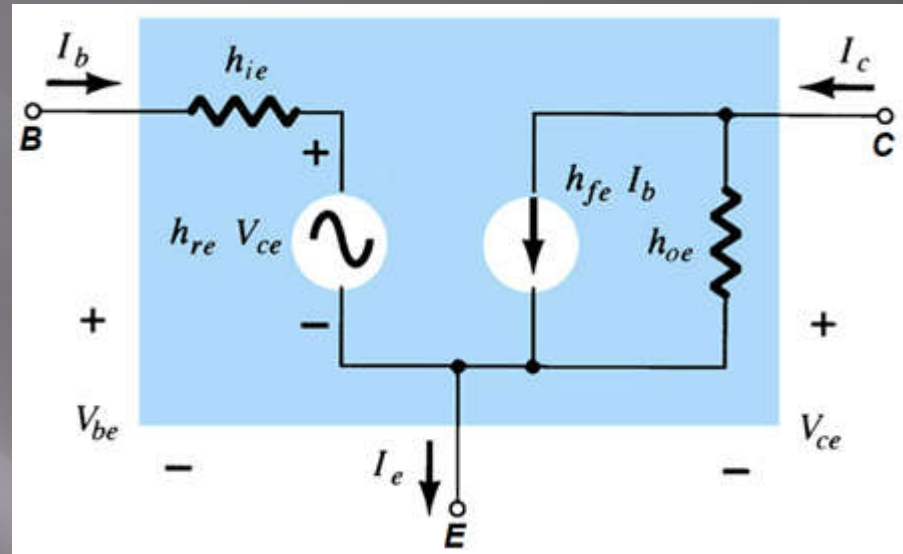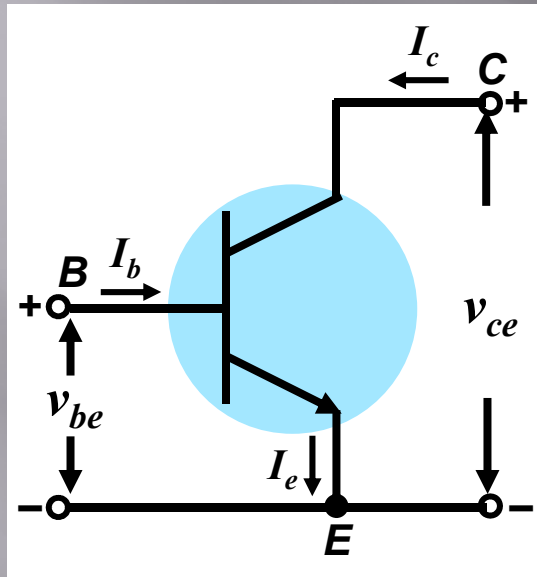

## CB $h$ -Parameter Equivalent Circuit

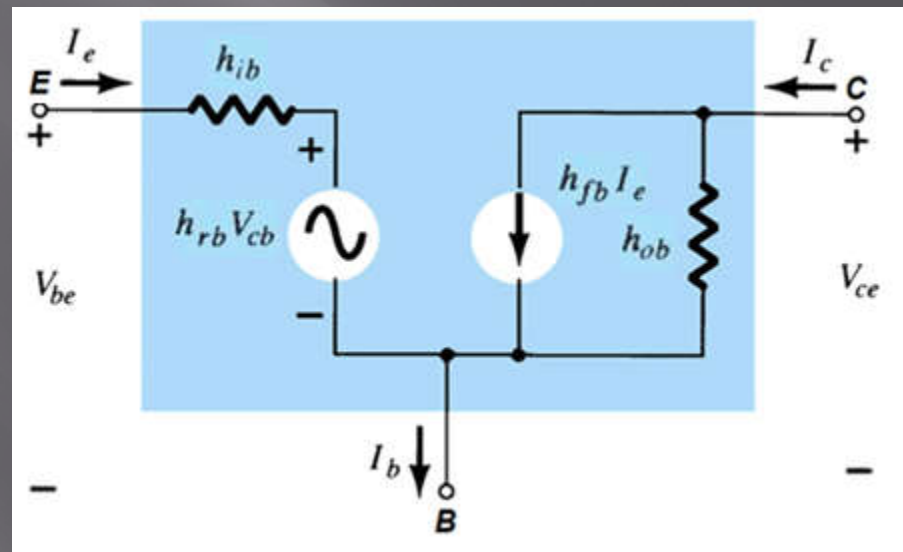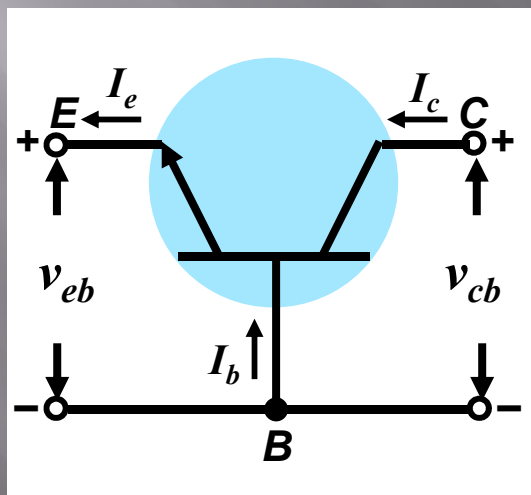


# CC $h$ -Parameter Equivalent Circuit

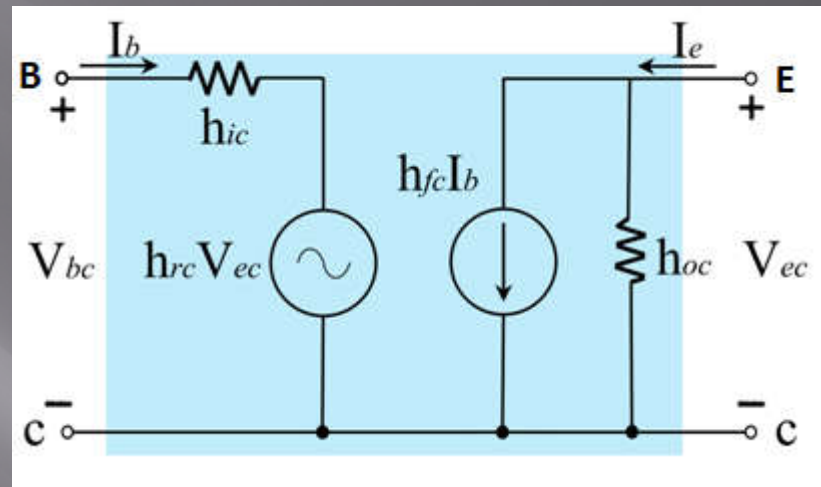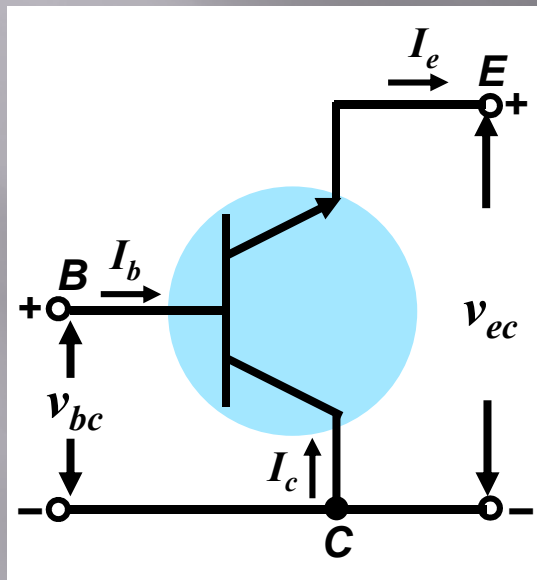


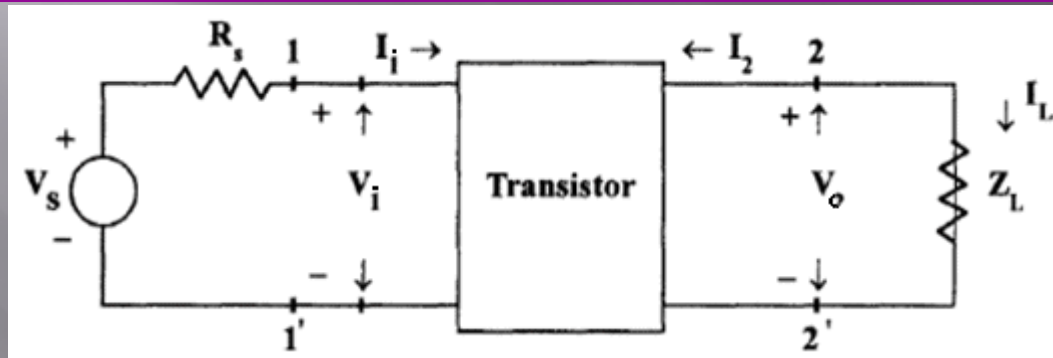
# Analysis of Transistor Amplifier using $h$ -Parameter Model

A basic amplifier circuit is shown in Fig. 1, where  $Z_L$  is the load resistance and  $R_s$  is the signal-source resistance.



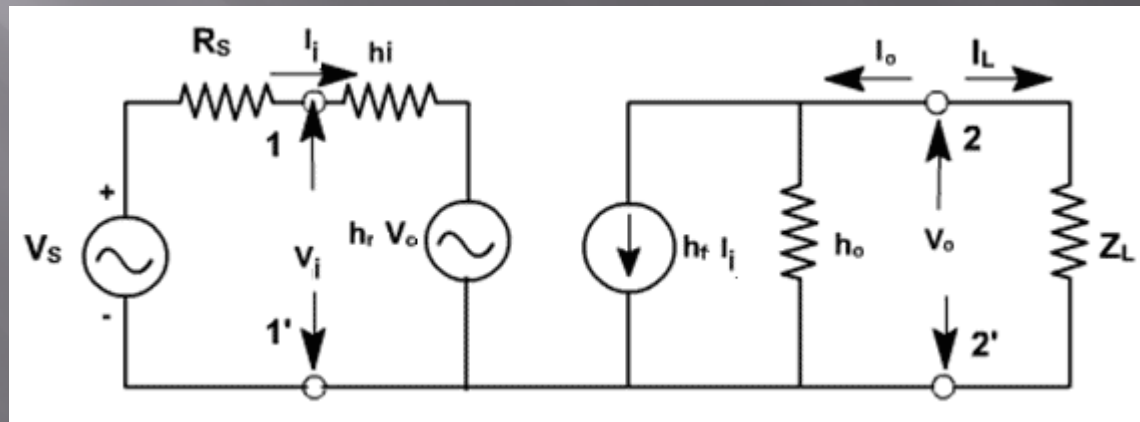Substituting the transistor with its  $h$ -parameter model, the above circuit is as shown in Fig. 2. It is assumed that  $h$ -parameters remain substantially constant over the operating range.



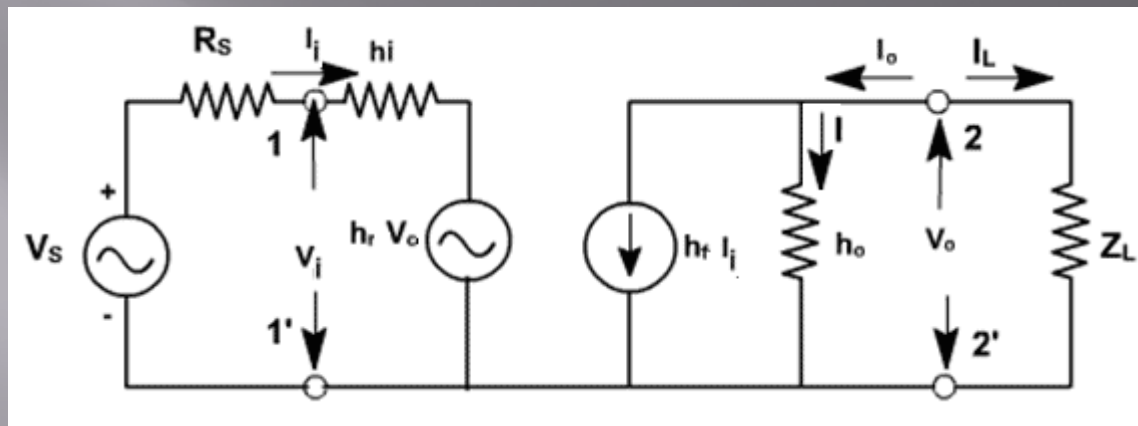

## Current Gain or Amplification Factor, $A_i$ :

For the transistor amplifier stage, current gain  $A_i$  is defined as the ratio of output current to input current and is given by:

$$A_i = \frac{I_L}{I_i} = \frac{-I_o}{I_i} \quad \dots \quad (ia)$$

From the circuit of Fig. 2, applying *KCL* to the node 2 of the output loop, yields

$$I_o = h_f I_i + I = h_f I_i + V_o h_o \quad \dots \quad (ib)$$


Substituting,  $V_o = -I_o Z_L$ , gives

$$I_o = h_f I_i - h_o Z_L I_o \quad \dots \quad (ic)$$

$$A_i = \frac{-I_o}{I_i} = \frac{-h_f}{1 + h_o Z_L} \quad \dots \quad (1)$$

so that,



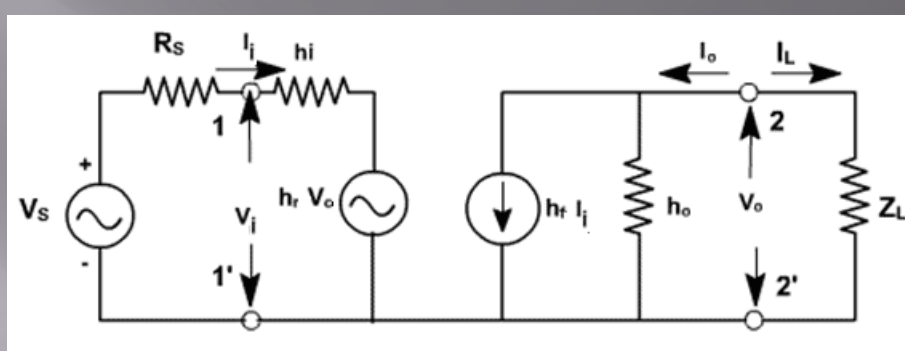

## Voltage Gain or Amplification Factor, $A_v$ :

Voltage gain  $A_v$  is defined as the ratio of output voltage to input voltage and is given by:

$$A_v = \frac{V_o}{V_i} \quad \dots \quad \text{(iia)}$$

From the circuit of Fig. 2, applying *KVL* to the input loop, results

$$V_i = h_i I_i + h_r V_o \quad \dots \quad \text{(iib)}$$

From (1),  $I_i = \frac{(1 + h_o Z_L) I_o}{h_f} = \frac{-(1 + h_o Z_L) V_o}{h_f Z_L} \quad \dots \quad \text{(iic)} \quad [\text{putting, } I_o = -V_o/Z_L]$


Substituting (iic) in (iib), results  $V_i = \frac{-(1 + h_o Z_L) h_i}{h_f Z_L} V_o + h_r V_o \quad \dots \quad \text{(iid)}$

Solving for  $V_o/V_i$ , yields

$$A_v = \frac{V_o}{V_i} = \frac{-h_o Z_L}{h_i + (h_i h_o - h_f h_r) Z_L} \quad \dots \quad \text{(2)}$$

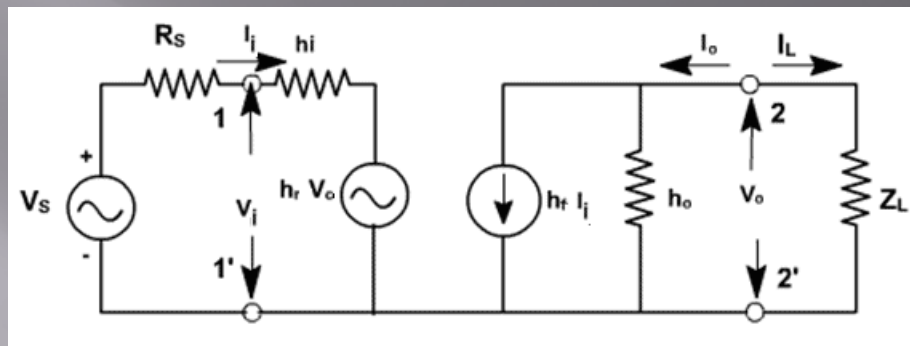Alternatively,  $A_v = \frac{V_o}{V_i} = \frac{-I_o Z_L}{V_i} = \frac{A_i I_i Z_L}{V_i} = \frac{A_i Z_L}{Z_i} \quad \dots \quad \text{(2a)}$





## Input Impedance, $Z_i$ :

The amplifier input impedance  $Z_i$  is the impedance seen looking into the input terminals (1, 1') and is given by:

$$Z_i = \frac{V_i}{I_i} \quad \dots \quad \text{(iiia)}$$


From the circuit of Fig. 2, applying *KVL* to the input loop, yields

$$V_i = h_i I_i + h_r V_o \quad \dots \quad \text{(iiib)}$$

Thus from (iiia),  $Z_i = \frac{h_i I_i + h_r V_o}{I_i} = h_i + \frac{h_r V_o}{I_i} \quad \dots \quad \text{(iiic)}$

Using (1),  $V_o = -I_o Z_L = A_i I_i Z_L$ , and then substituting  $V_o$  in (iiic), results
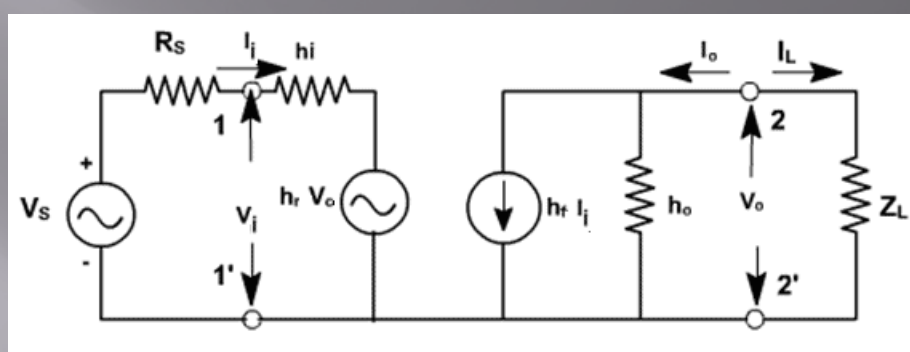
$$Z_i = h_i + h_r A_i Z_L = h_i - \frac{h_r h_o Z_L}{1 + h_o Z_L} \quad \dots \quad \text{(3)}$$



## Output Impedance, $Z_o$ and Admittance $Y_o$ :


By definition, the amplifier output impedance  $Z_o$  is obtained by setting the source voltage  $V_s$  to zero load impedance to infinity and driving the output terminals (2, 2') from a generator voltage  $V_o$ . If the current drawn from the generator ( $V_o$ ) is  $I_o$ , thus  $Z_o = \frac{V_o}{I_o} \dots \dots$  (iva) with  $V_s = 0$  and  $Z_L = \infty$

From the circuit of Fig. 2, putting  $V_s = 0$  and applying KCL to the input loop, yields  $R_s I_i + h_i I_i + h_r V_o = 0$   
or,  $I_i = \frac{-h_r V_o}{R_s + h_i} \dots \dots$  (ivb)

From the output loop of the circuit of Fig. 2,  $I_o = h_f I_i + h_o V_o = \frac{-h_f h_r V_o}{R_s + h_i} + V_o \dots \dots$  (ivc)

Hence,  $Z_o = \frac{V_o}{I_o} = \frac{1}{h_o - h_f h_r / (R_s + h_i)} \dots \dots$  (4)  $Y_o = \frac{1}{Z_o} = h_o - \frac{h_f h_r}{(R_s + h_i)} \dots \dots$  (4a)

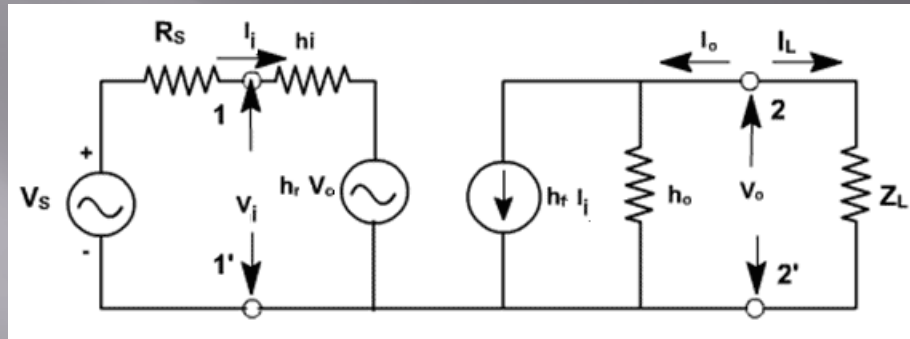Note that output impedance/admittance is a function of source resistance.



## Power Gain or Amplification Factor, $A_p$ :

The average output power delivered to the load is given by:

$$P_L = V_L I_L = V_o I_o$$

The input power supplied by the source is:


$$P_i = V_i I_i$$

Therefore, power gain  $A_p$  is given by:

$$A_p = \frac{V_o I_o}{V_i I_i} = A_v A_p$$

In terms of  $h$ -parameters, using (1) and (2)
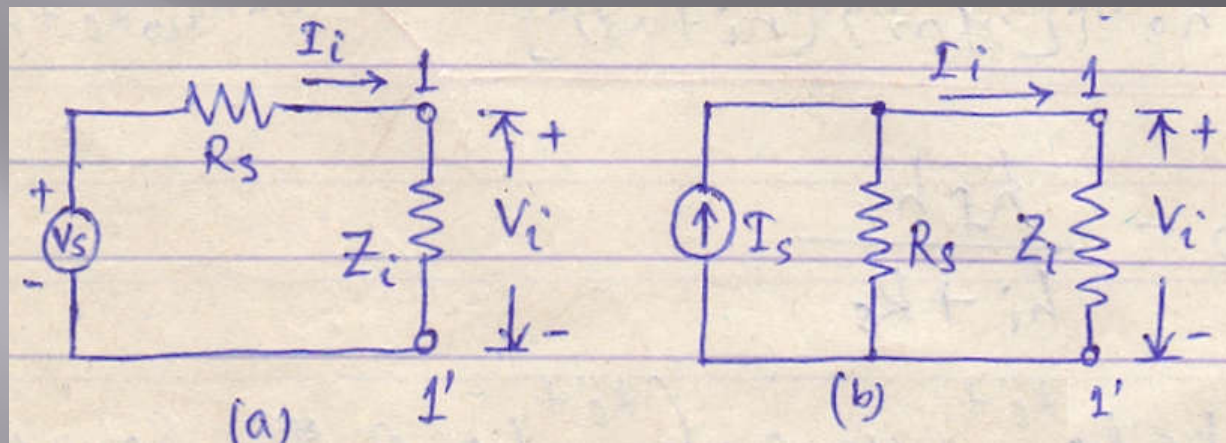
$$A_p = \frac{h_f^2 Z_L}{(1 + h_o Z_L)[h_i + (h_i h_o - h_f h_r) Z_L]} \dots \dots (5)$$



## Voltage Gain or Amplification Factor, $A_{vs}$ (taking in account the Source Resistance $R_s$ ):

This overall voltage gain  $A_{vs}$  is defined by:

$$A_{vs} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \frac{V_i}{V_s} = A_v \frac{V_i}{V_s} \quad \dots \quad (i)$$


From the equivalent input circuit of the amplifier shown in Fig. 3(a):

$$V_i = Z_i I_i = Z_i \frac{V_s}{Z_i + R_s} \quad \dots \quad (ii)$$

Hence,  $A_{vs} = A_v \frac{V_i}{V_s} = A_v \frac{Z_i}{Z_i + R_s} = \frac{A_i Z_L}{Z_i} \frac{Z_i}{Z_i + R_s} = \frac{A_i Z_L}{Z_i + R_s} \quad \dots \quad (6) \quad [\text{using (2a)}]$

For an ideal voltage source,  $R_s = 0$ , then  $A_{vs} = A_v$ .

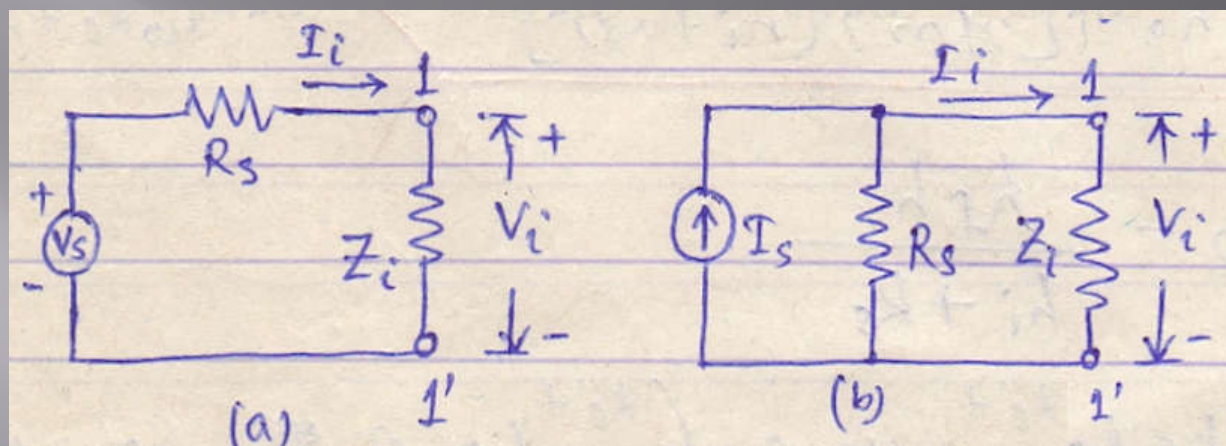In practice,  $R_s \neq 0$ , thus,  $A_{vs}$  is less than  $A_v$ .



### Current Gain or Amplification Factor, $A_{is}$ (taking in account the Source Resistance $R_s$ ):

Converting the voltage source into its equivalent current source as shown in Fig. 3(b), then this overall current gain  $A_{is}$  is defined by:

$$A_{is} = \frac{-I_0}{I_s} = \frac{-I_0}{I_i} \frac{I_i}{I_s} = A_i \frac{I_i}{I_s} \quad \dots \quad (i)$$

From Fig. 3(b):

$$I_i = \frac{V_i}{Z_i} = \frac{I_s (R_s \parallel Z_i)}{Z_i} = \frac{I_s}{Z_i} \left( \frac{R_s Z_i}{Z_i + R_s} \right) = \frac{I_s R_s}{Z_i + R_s} \quad \dots \quad (ii)$$

Hence,

$$A_{is} = A_i \frac{I_i}{I_s} = A_i \frac{R_s}{Z_i + R_s} \quad \dots \quad (7)$$

For an ideal current source,  $R_s = \infty$ , then  $A_{is} = A_i$ .


Thus, taking source resistance into account, the voltage and current gains are related by

$$A_{vs} = A_{is} \frac{Z_L}{R_s} \quad \dots \quad (8)$$




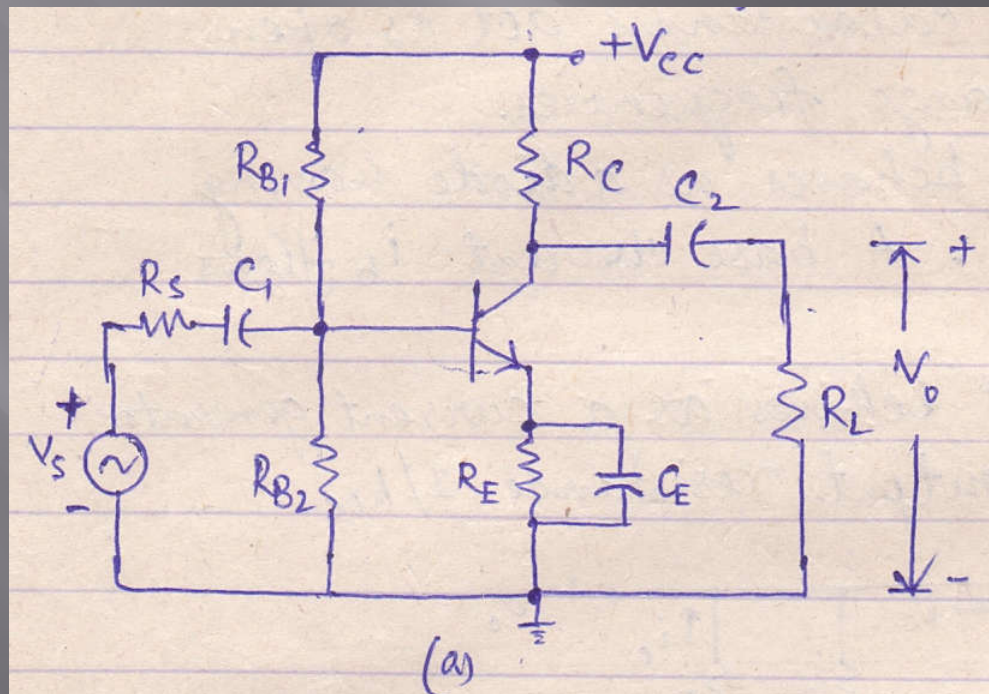
# Analysis of BJT CE Amplifier using $h$ -Parameter Model

A BJT common-emitter ac amplifier is shown in Fig. (a). Resistor  $R_s$  is added to control the input current from the source  $V_s$ , and resistor  $R_L$  represents the load as seen by the amplifier.






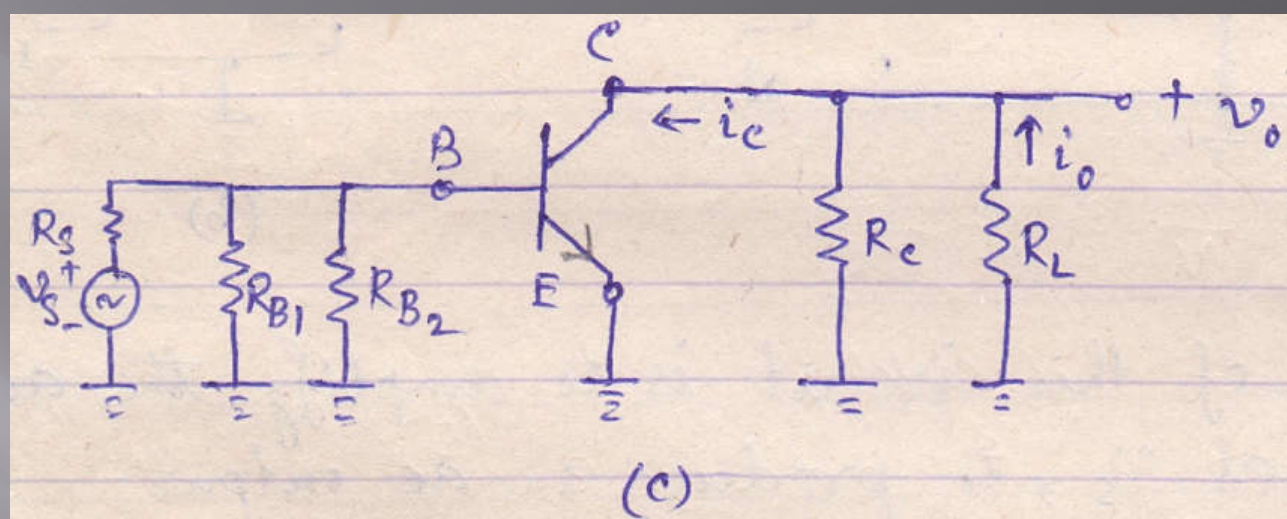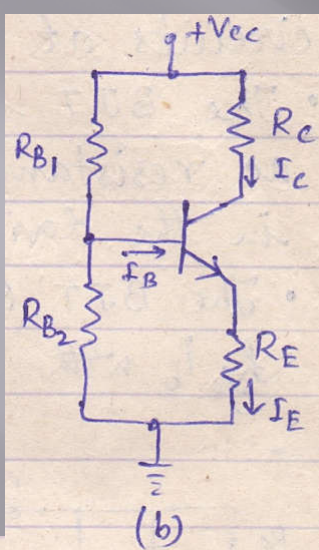

The purpose of this circuit is to amplify the ac input signal  $v_s$ , to produce an ac output signal  $v_o$  that is larger in amplitude. The capacitors act as short circuits for the mid-range frequencies. Resistors  $R_{B1}$ ,  $R_{B2}$ ,  $R_C$ , and  $R_E$  provide the dc bias so that the BJT operates in the linear region [Fig. (b)].

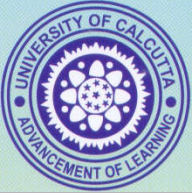The small signal ac equivalent circuit of fig. (a) is drawn in fig. (c). In order to develop






In order to develop fig. (c), the following observations and assumptions are made:

- Any node whose voltage is constant in time is considered to be ac ground. The resistance of all supplies is assumed negligible with respect to circuit parameters, so power supply nodes are ac ground.
- $C_1$ ,  $C_2$ , and  $C_E$  act as short circuit at mid-range frequencies.
- Device and wiring capacitances act as open circuits at midrange frequencies.
- The BJT input behaves as a diode having ac resistance  $h_{ie}$ . A base current  $i_b$  flows in the device.
- The BJT output behaves as a current generator  $h_{fe} i_b$  with an output resistance  $1/h_{oe}$ .



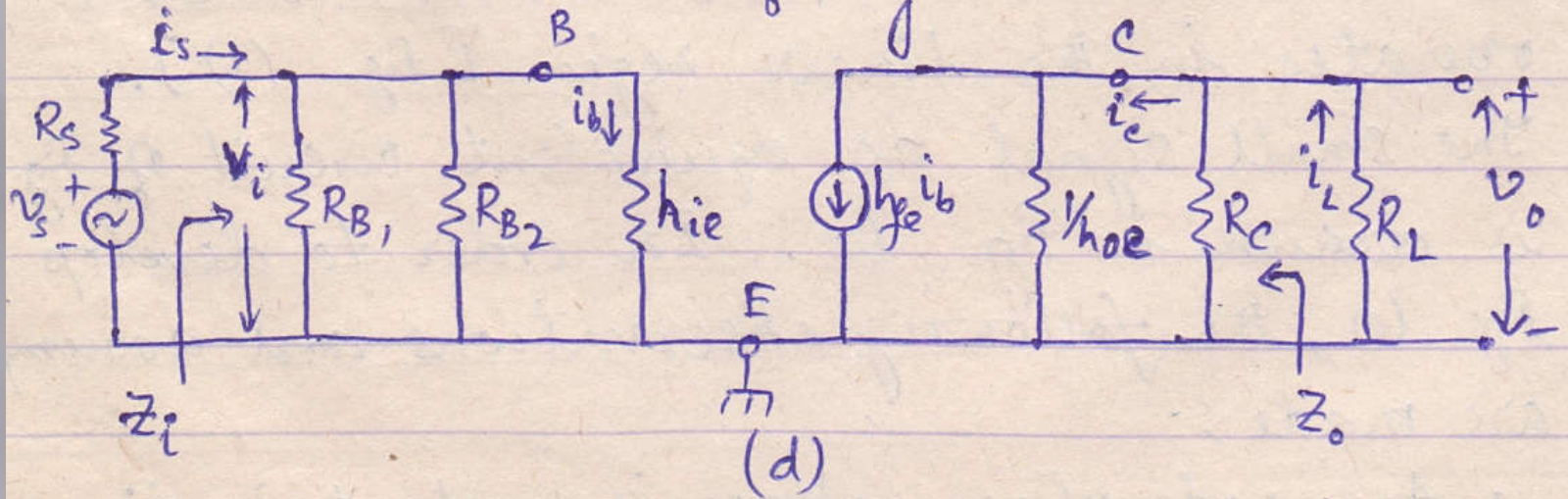Substituting the approximate hybrid small-signal equivalent circuit for the transistor of fig. will result in the network of fig.




Input impedance  $Z_i$  :

The input impedance is given by

$$Z_i = R_{B1} \parallel R_{B2} \parallel h_{ie} \quad \dots (1)$$


Output impedance  $Z_o$ :

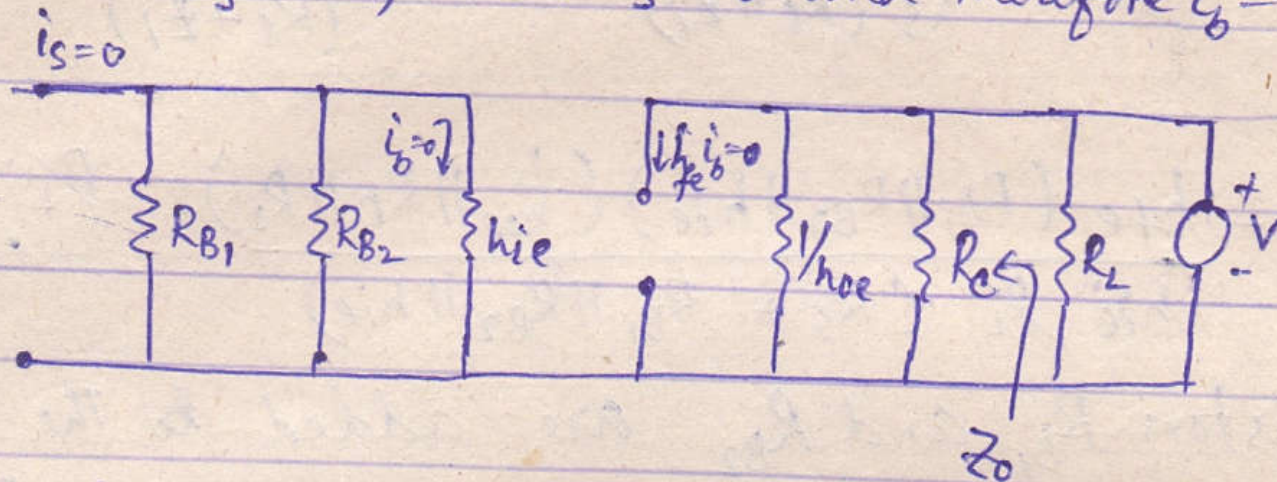When  $V_s = 0$ , then  $i_s = 0$  and therefore  $i_b = 0$  and  $i_e = 0$ .



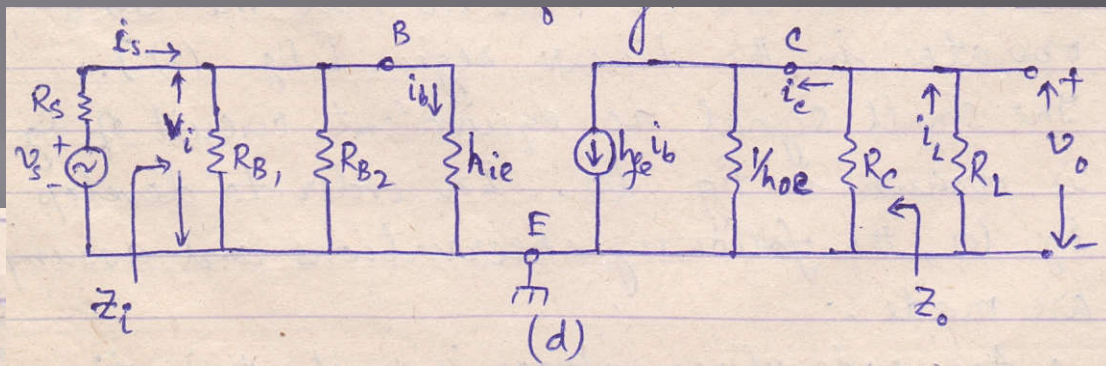Thus,  $Z_o = \frac{1}{h_{oe}} \parallel R_c \dots (2)$





Current Gain  $A_i$  :

$$A_i = \frac{i_L}{i_s} = \frac{i_L}{i_b} \cdot \frac{i_b}{i_s}$$

from fig.  $v_i = i_s (R_{B1} \parallel R_{B2} \parallel h_{ie}) = i_b h_{ie}$

$$\therefore \frac{i_b}{i_s} = \frac{R_{B1} \parallel R_{B2} \parallel h_{ie}}{h_{ie}}$$


and  $-v_o = i_L R_L = h_{fe} i_b (\frac{1}{h_{oe}} \parallel R_C \parallel R_L)$

$$\therefore \frac{i_L}{i_b} = \frac{h_{fe} (\frac{1}{h_{oe}} \parallel R_C \parallel R_L)}{R_L}$$

So the current gain of the circuit becomes
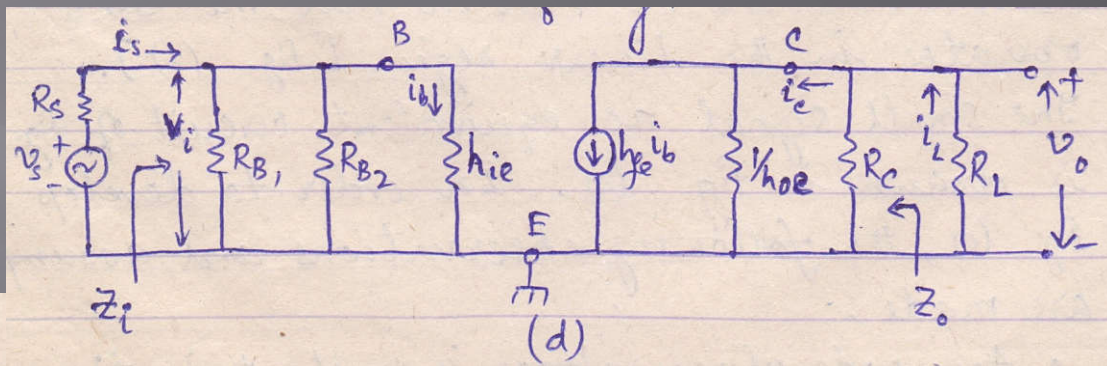
$$A_i = h_{fe} \frac{(R_{B1} \parallel R_{B2} \parallel h_{ie})}{h_{ie}} \frac{(\frac{1}{h_{oe}} \parallel R_C \parallel R_L)}{R_L} \dots (3)$$





Voltage Gain  $A_v$ :

From fig.

$$v_o = -i_L R_L = -h_{fe} i_b \left( \frac{1}{h_{oe}} \parallel R_c \parallel R_L \right)$$

and  $v_s = i_s (R_s + Z_i)$

so the voltage gain of the circuit is given by

$$\therefore A_v = \frac{v_o}{v_s} = \frac{-i_L R_L}{i_s (R_s + Z_i)} = -A_i \frac{R_L}{(R_s + Z_i)}$$

$$\text{or, } A_v = \frac{-h_{fe} (R_{B1} \parallel R_{B2} \parallel h_{ie}) \left( \frac{1}{h_{oe}} \parallel R_c \parallel R_L \right) \cdot R_L}{h_{ie} R_L (R_s + R_{B1} \parallel R_{B2} \parallel h_{ie})} \quad \dots (4)$$




Note: Resistors  $R_{B1}$  and  $R_{B2}$  are added to the amplifier to improve the thermal stability of the circuit. The following effects are associated with these resistors:

- The input impedance  $Z_i$  of the amplifier is reduced.
- The current gain  $A_i$  of the amplifier is reduced.
- The voltage gain of the amplifier is approximately unchanged for the case  $R_S \ll (R_{B1} \parallel R_{B2} \parallel h_{ie})$ . Otherwise,  $A_v$  also is reduced.

For a special case, if  $R_{B1}$  and  $R_{B2} \gg h_{ie}$ , and  $1/h_{oe}$  and  $R_L \gg R_C$ , then
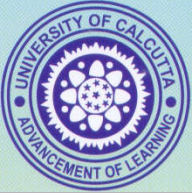
$$A_v = - h_{fe} \cdot \frac{R_C}{R_S + h_{ie}} \quad \dots (5)$$





Example: A CE amplifier uses a transistor with  $h_{ie} = 1100 \Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$ ,  $h_{fe} = 50$ , and  $h_{oe} = 25 \times 10^{-6} S$ . If  $R_L = 10k$  and  $R_s = 1k$ , find the various gains and the input and output impedances.

Solution:

$$A_I = -\frac{h_{fe}}{1 + h_{oe} R_L} = -\frac{50}{1 + 25 \times 10^{-6} \times 10^4} = -40$$

$$R_i = h_{ie} + h_{re} A_I R_L = 1100 + 2.5 \times 10^{-4} \times 40 \times 10^4 = 1000 \Omega = 1k$$

$$A_V = \frac{A_I R_L}{R_i} = -\frac{40 \times 10}{1} = -400$$

$$A_V = \frac{A_I R_L}{R_i} = -\frac{40 \times 10}{1} = -400$$


$$A_{Vs} = \frac{A_V R_i}{R_i + R_s} = \frac{-400 \times 1}{1 + 1} = -200$$

$$A_{fs} = \frac{A_I R_s}{R_i + R_s} = \frac{-40 \times 1}{1 + 1} = -20$$

$$\begin{aligned} Y_o &= h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s} = 25 \times 10^{-6} - \frac{50 \times 2.5 \times 10^{-4}}{1100 + 1000} \\ &= 19 \times 10^{-6} S = 19 \mu A/V \end{aligned}$$
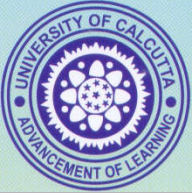
$$\text{or, } Z_o = \frac{1}{Y_o} = \frac{10^6}{19} \Omega = 52.6k$$





## Example

The ~~transistor~~ A CE amplifier uses a transistor with  $h_{ie} = 1\text{k}\Omega$ ,  $h_{re} = 5 \times 10^{-4}$ ,  $h_{fe} = 100$ , and  $h_{oe} = 25 \times 10^{-6} \text{ S}$ . The load resistance is  $5\text{k}\Omega$  and <sup>the source resistance is  $1\text{k}\Omega$</sup>  find the current amplification, and find the various gains and the input and output impedances.

Solution:

$$A_I = - \frac{h_{fe}}{1 + h_{oe} R_L} = - \frac{100}{1 + 25 \times 10^{-6} \times 5 \times 10^3} = -88.89$$

$$R_i = h_{ie} + h_{re} A_I R_L = 10^3 - 88.89 \times 5 \times 10^{-4} \times 5 \times 10^3 = 777.8 \Omega$$

$$A_V = A_I \frac{R_L}{R_i} = -88.89 \times \frac{5 \times 10^3}{777.8} = -$$

$$A_{Vs} = \frac{A_V R_i}{R_i + R_s} = \frac{A_I R_L}{R_i + R_s} = - \frac{88.89 \times 5 \times 10^3}{10^3 + 777.8} = -250$$

$$Y_o = h_{oe} - \frac{h_{fe} h_{re}}{h_{ie} + R_s} = 25 \times 10^{-6} - \frac{100 \times 5 \times 10^{-4}}{5 \times 10^3 + 1 \times 10^3}$$
$$A_{Is} = \frac{A_I R_s}{h_{ie} + R_s}$$



$$Z_o = \frac{1}{Y_o} =$$

$$A_{Po} = A_{Vo} A_{Io} =$$



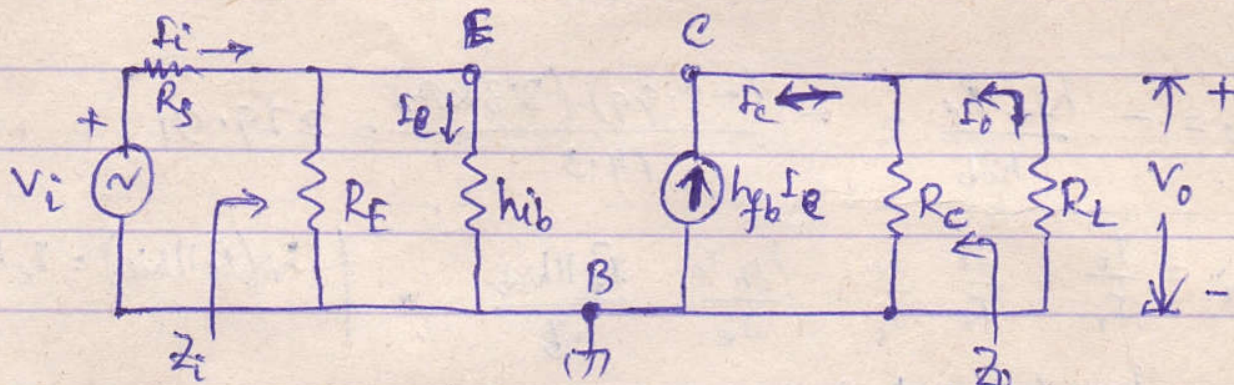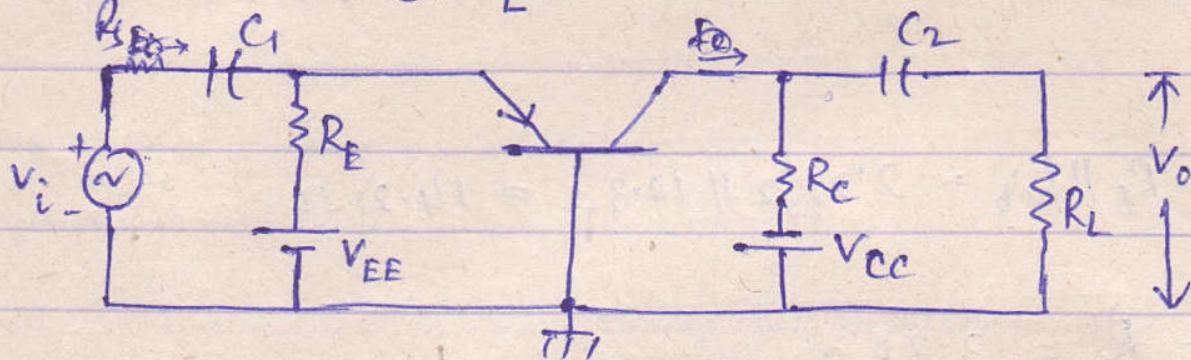
## BJT Common-Base Amplifier

A BJT common-base circuit, its dc portion, and its h-parameter (approximate) ac equivalent are shown in fig. In this configuration, the output resistance  $1/h_{ob}$  is usually sufficiently large to neglect its impact on  $R_E \parallel R_L$ .





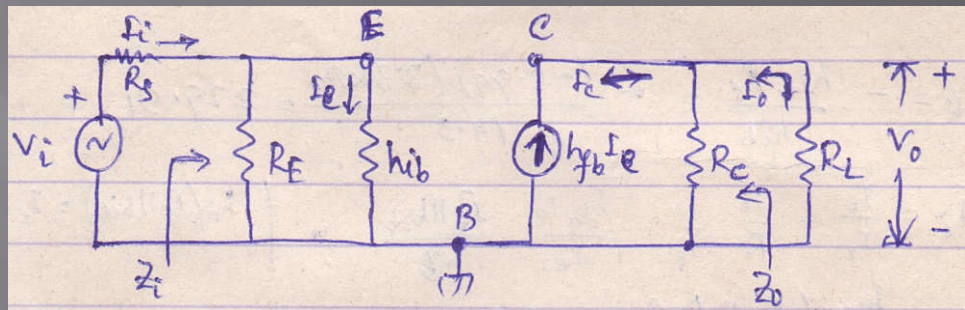

$$Z_i: Z_i = R_E \parallel h_{ie}$$

$$Z_o: Z_o = R_c$$

$$A_v: V_o = -I_o R_L = -h_{fe} I_e (R_c \parallel R_L)$$


$$V_i = I_i (R_s + Z_i) = \frac{h_{ie} I_e}{Z_i} (R_s + Z_i)$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{-h_{fe} (R_c \parallel R_L)}{h_{ie}} \cdot \frac{Z_i}{(R_s + Z_i)} = -\frac{h_{fe}}{h_{ie}} \left( \frac{Z_i}{R_s + Z_i} \right) (R_c \parallel R_L)$$

$$A_i: A_i = \frac{I_o}{I_i} = \frac{I_o}{I_e} \cdot \frac{I_e}{I_i} = \frac{h_{fe} (R_c \parallel R_L)}{R_L} \cdot \frac{Z_i}{h_{ie}} = \frac{h_{fe}}{h_{ie}} \cdot \frac{Z_i}{R_L} (R_c \parallel R_L)$$

Example: For the network of Fig. determine:

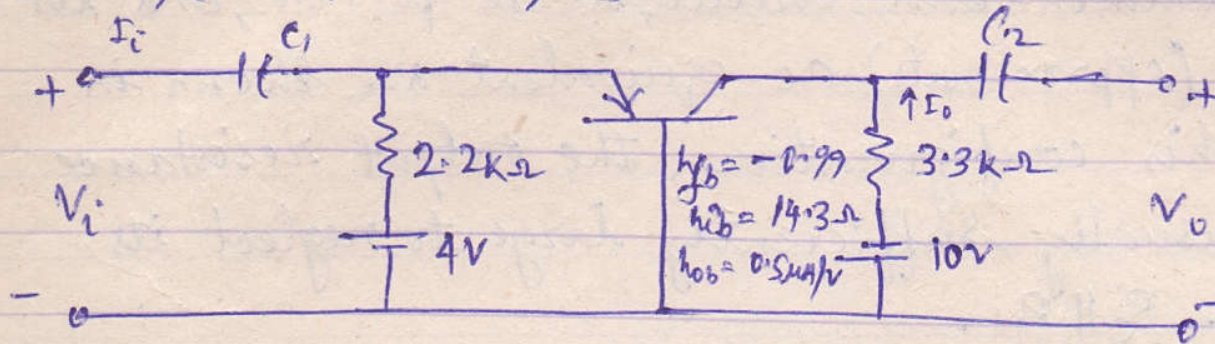(a)  $Z_i$ ; (b)  $Z_o$ ; (c)  $A_v$ ; (d)  $A_i$ .



Solution: (a)  $Z_i = R_E \parallel h_{ie} = 2.2k\Omega \parallel 14.3\Omega = 14.21\Omega$

(b)  $Z_o = R_E = 3.3k\Omega$

(c)  $A_v = - \frac{h_{fb} R_E}{h_{ie}} = - \frac{(-0.99)(3.3k\Omega)}{14.3} = 229.91$


(d)  $A_i = \frac{I_o}{I_i} = \frac{I_o}{I_e} \cdot \frac{I_e}{I_i} = \frac{h_{fb} I_e}{I_e} \cdot \frac{R_E \parallel h_{ie}}{h_{ie}} \quad \left| \quad I_i(R_E \parallel h_{ie}) = I_e h_{ie} \right.$   
 $= \frac{h_{fb}}{h_{ie}} (R_E \parallel h_{ie}) = \frac{-0.99}{14.3\Omega} \times 14.21\Omega = -1$






# Three Small signal Models of CE Transistor

## The Mid-frequency small-signal models

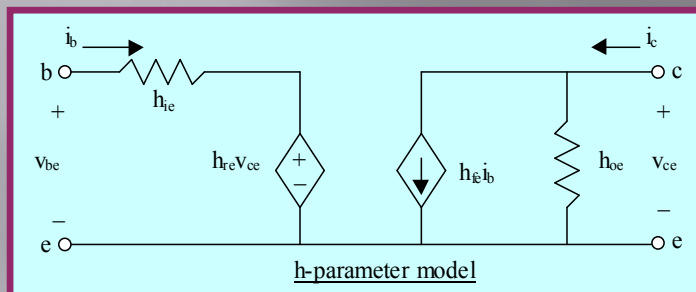

Alternate names:
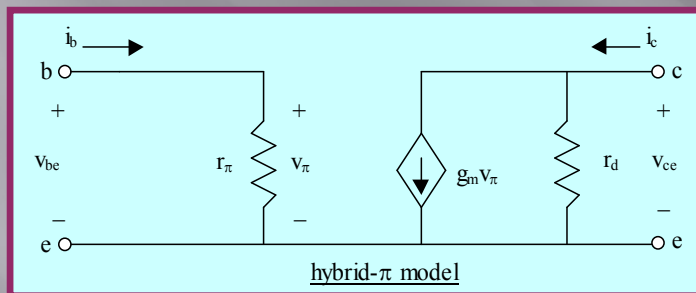
$$h_{fe} = \beta_{ac} = \beta_o = \beta$$




$$g_m = \frac{38.92}{n} |I_C| \quad (\text{Note: Uses DC value of } I_C)$$

where  $n = 1$  (typical, Si BJT)

$$\beta_o = h_{fe} \quad r_d = \frac{1}{h_{oe}}$$
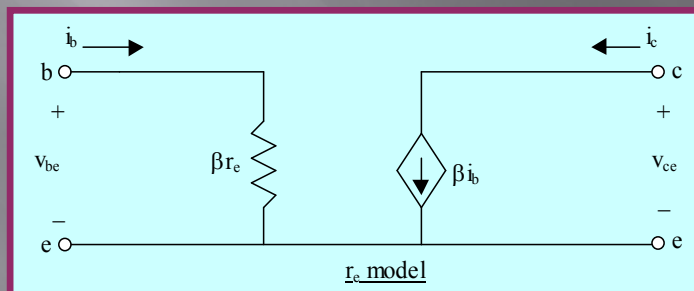
$$h_{re} = 0 \quad r_\pi = h_{ie} = \frac{\beta_o}{g_m}$$



$$r_e = \frac{26 \text{ mV}}{I_B} \quad (\text{Note: uses DC value of } I_B)$$

$$\beta_o = h_{fe}$$

$$\beta_o r_e = h_{ie}$$

$$h_{re} = 0$$

$$h_{oe} = 0, \text{ or use } r_d = \frac{1}{h_{oe}}$$

THANK YOU